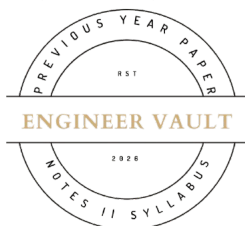


Total No. of Printed Pages:01



SUBJECT CODE NO: - RNP-8018
FACULTY OF SCIENCE AND TECHNOLOGY
S.E (EEE / EE / EEP) (NEP) Sem - III
Examination May/June-2026
Electronics Devices & Circuits

[Time: 1:30 Hours]**[Max. Marks: 30]**

N. B

Please check whether you have got the right question paper.

1. Part A: Question No 1 is compulsory.
2. Attempt any FOUR questions from Part B: Q.2 to Q.7.
3. Use of non-programmable calculator is allowed

Part A**Q.1 Attempt ANY FIVE of the following questions****10**

- a) In a PN junction diode, the width of depletion layer increases during:
 - i) Forward bias
 - ii) Reverse bias
 - iii) Zero bias only
 - iv) High temperature only
- b) Define Q point & DC load line in BJT with suitable diagrams
- c) Define a Frequency response & Bandwidth of an amplifier
- d) Peak Inverse Voltage (PIV) of a diode is:
 - i) Maximum forward voltage
 - ii) Maximum reverse voltage it can withstand
 - iii) Average output voltage
 - iv) RMS voltage
- e) Draw the symbols of Diode, BJT, FET & MOSFET
- f) State the Bark Husain Criteria for Oscillations
- g) Match the pairs:

Sr. No.	Parameters	Sr. No.	Options
1	BJT	a	Ripples remover
2	FET	b	AC to DC
3	Filter	c	Voltage controlled
4	Rectifier	d	Current controlled

Part B**Attempt ANY FOUR of the following questions**

- Q.2** Explain the Block diagram of DC regulated Power Supply **05**
- Q.3** Define a Rectifier and explain all types of rectifiers with input & output waveforms. **05**
- Q.4** Draw the circuit diagram of BJT based RC coupled amplifier **05**
- Q.5** Define BJT Biasing? State the types of Biasing & explain any one **05**
- Q.6** Differentiate between BJT, FET & MOSFET **05**
- Q.7** Write a detailed note on High frequency oscillators **05**

