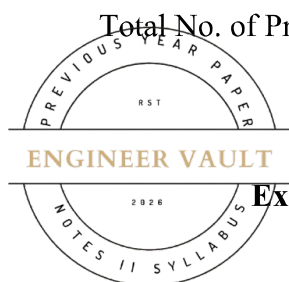


Total No. of Printed Pages: 1



SUBJECT CODE NO: - RNP-8023
FACULTY OF SCIENCE AND TECHNOLOGY
S.E (EEE / EE / EEP) (NEP) Sem - III

Examination November / December 2025 (To be held in February-2026)

Electronics Devices & Circuits

[Time: 2 Hours]**[Max. Marks: 30]**

Please check whether you have got the right question paper.

N. B

- 1) Part A: Question No 1 is compulsory.
- 2) Attempt any FOUR questions from Part B: Q.2 to Q.7.
- 3) Use of non-programmable calculator is allowed

Part A**Q1 Attempt ANY FIVE of the following questions****10**

- a) Draw the Symbols BJT, FET & MOSFET
- b) Define Load Regulation & Line Regulation
- c) Draw the Drain & Transfer Characteristics of N-Channel FET"
- d) State the Barkhausen Criteria for Oscillations
- e) Match the pairs:

Sr. No.	Parameters	Sr. No.	Options
1	Crystal Oscillator	a	Removes Ripple
2	Voltage Divider Circuit	b	Produces High frequency signal
3	Voltage Multiplier	c	Universal Biasing
4	Filter circuit	d	Converts low AC to high DC voltage

- f) State the advantages & Disadvantages of negative feedback
- g) Define oscillator with Block diagram

Part B

- Q. 2** Draw & Explain the Block diagram of DC regulated Power Supply, with wave-forms **5**
- Q. 3** Define a Filter and explain all types of filters with input & output waveforms. **5**
- Q. 4** Draw & Explain the circuit diagram of BJT based RC coupled amplifier **5**
- Q. 5** What is BJT Biasing? State the types of Biasing & explain any one type **5**
- Q. 6** Define an FET. Explain working of N-Channel FET with suitable diagrams **5**
- Q. 7** Define an oscillator? Explain Colpitt's Oscillator in details **5**

